

# Sequential Logic circuits

# Introduction to Sequential Logic Circuits

Sequential logic circuit are the Digital circuits where output is determined by the present input and past inputs

These type of circuits contains memory as feedback and sequence of inputs determines the output


E.g., flip-flops, data storage cells in registers, memory, counters, & control logic in processor

Therefore, these circuits produce different outputs for the same set of inputs **depending on what is stored in memory**


# Block diagram of a sequential logic circuit

- Main features

 1. At least one feedback path from the input to the output of the system
2. System has memory capability to hold past inputs
3. The circuits that output depends to inputs only known as combinational logic circuits where for sequential logic circuit's output depends on not only inputs but also the past outputs




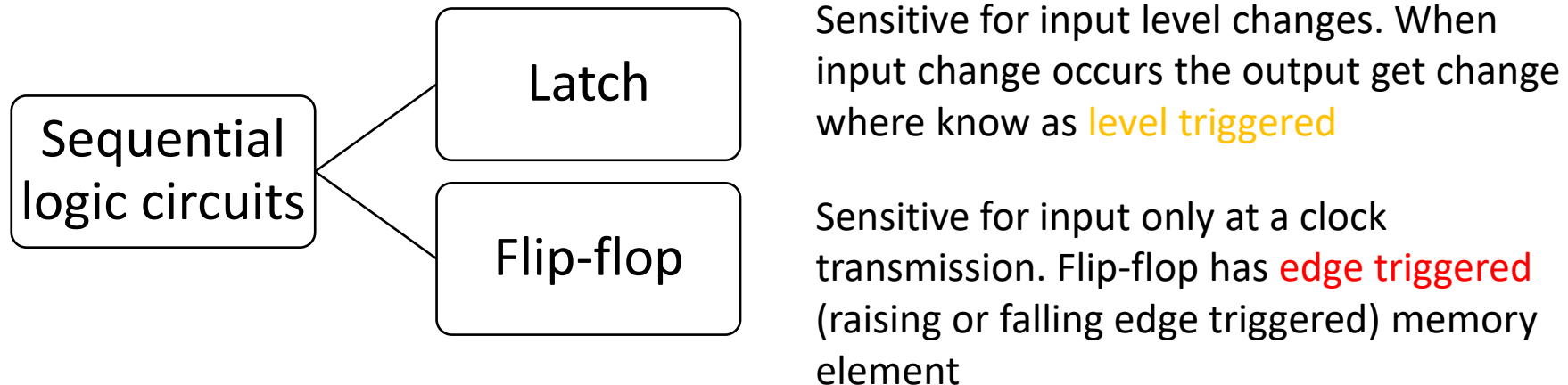- Sequential logic circuits are basically two types
  - Synchronous logic circuit- Response to the input when **discrete time intervals**
  - Asynchronous logic circuit- Response to the input only at **input level change**


 
# Latch



- A latch is a data storage (memory) device that can store **one bit** of information.
- The basic type of Latch is two NOT gate Latch
- A logic gate itself doesn't have an ability to hold a logic value rather than passing the logic through logic gate
- Combination of two logic gates has an ability to hold a logic value and act as a memory



# Latch

- Latches are basically two types
  - NOR Gate Latch
  - NAND Gate Latch

# NOR Gate Latch

  

R	S	Q	Action
0	0	Last Value	No Change
0	1	1	Set
1	0	0	Reset
1	1	?	Not Allowed


Truth table with all states :



S	R	Q <sub>n</sub>	$\overline{Q}_n$	Q <sub>n+1</sub>	$\overline{Q_{n+1}}$
0	0	0	1	0	1
		1	0	1	0
0	1	0	1	0	1
		1	0		
1	0	0	1	1	0
		1	0		
1	1	0	1	Not allowed	
		1	0		


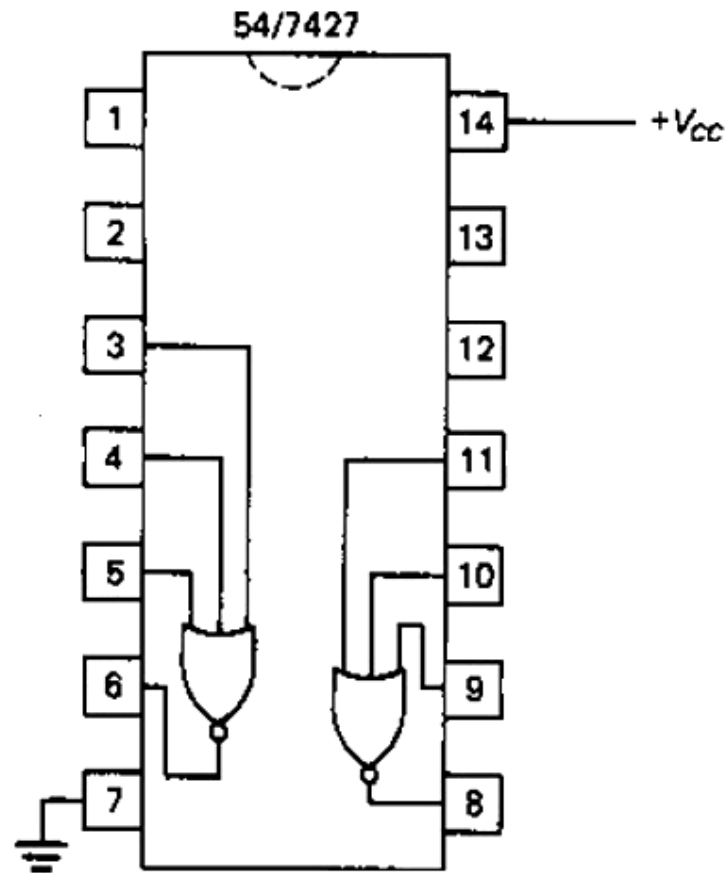
## EXAMPLE

Use the pinout diagram for a 54/7427 triple 3-input NOR gate and show how to connect a simple *RS* flip-flop.



 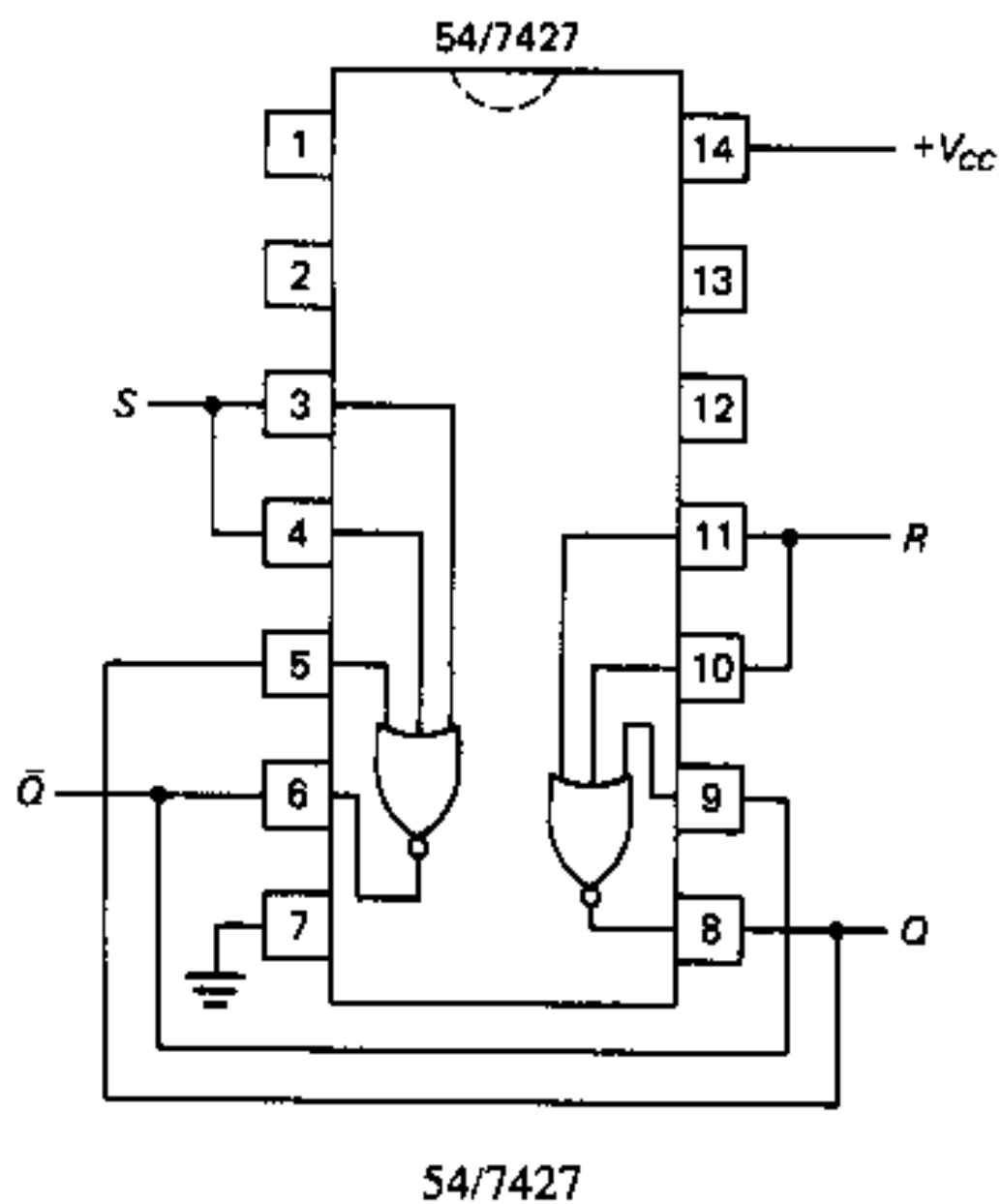


(a) Logic symbol

$R$	$S$	$Q$
0	0	Last state
0	1	1
1	0	0
1	1	? (Forbidden)

(b) Truth table


RS flip-flop

# NAND Gate Latch

 

(a) NAND gate latch

$\bar{R}\bar{S}$  flip-flop

 

(b) Logic symbol

$\bar{R}$	$\bar{S}$	$Q$
1	1	Last state
1	0	1
0	1	0
0	0	? (Forbidden)


(c) Truth table

# EXAMPLE


Show how to convert the  $\overline{R}\overline{S}$  flip-flop into an  $RS$  flip-flop.

Solution:

 By placing an inverter at each input shown in figure below, 2 inputs are now  $R$  and  $S$ , and resulting circuit behaves exactly as the  $RS$  flip-flop



(a) 54/7400

 

(b) Symbol

$R$	$S$	$Q$
0	0	Last state
0	1	1
1	0	0
1	1	? (Forbidden)

(c)

An  $RS$  flip-flop (latch)


# Flip – Flop

Flip Flops can change it's state continues either 0 Or 1 logic levels

A Clock cycle has been provided additionally with the inputs of the flip – flops where it differs from Latches

Continues logic level changing occurs when input got triggered with a clock cycles

 There are level triggered and edge triggered (rising or falling edge) flip flops according to the clock cycles




# Types of Clock Cycles

**50% duty cycle**



Equal time of on and off time

**75% duty cycle**

 

Raising time is high falling time is low

**25% duty cycle**



Raising time is low falling time is high

In Physically clock cycles are provided by 555 timer IC's



# Type of Flip- Flops

- SR Flip Flop
- JK Flip Flop
- D- Flip Flop
- T – Flip Flop

# S-R Flip Flop

Truth Table

S	R	$Q_{n-1}$
0	0	$Q_n$
0	1	0 (Reset)
1	0	1 (Set)
1	1	Not allowed

  

Excitation Table

$Q_n$		S	R
0	0	0	0
		0	1
0	1	1	0
1	0	0	1
1	1	0	0
		1	0



$Q_n$		S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0




# SR Flip Flop with NAND Gate


CK	S	R	$Q_{n+1}$
0	0	0	$Q_n$
0	0	1	$Q_n$
0	1	0	$Q_n$
0	1	1	$Q_n$
1	0	0	$Q_n$
1	0	1	0
1	1	0	1
1	1	1	NA

When CK is low  $Q_{n+1} = Q_n$

Clk	S	R	$Q_n$
0	X	X	$Q_{n-1}$
1	0	0	$Q_{n-1}$
1	0	1	0
1	1	0	1
1	1	1	X

 


# SR Flip Flop NOR Gate

 


Clk	S	R	$Q_n$
0	X	X	$Q_{n-1}$
1	0	0	$Q_{n-1}$
1	0	1	0
1	1	0	1
1	1	1	X

 Draw the output waveform for the (+)ve edge triggered SR FF



# JK Flip- Flop

 

Truth Table


J	K	$Q_n$
0	0	$Q_{n-1}$
0	1	0
1	0	1
1	1	$Q_{n-1}'$

Excitation Table


$Q_n$	J	K
0	0	0
	0	1
0	1	0
	1	1
1	0	1
	1	1
1	1	0
	1	0



$Q_n$	J	K
0	0	X
0	1	X
1	0	1
1	1	0

 


# D Flip - Flop

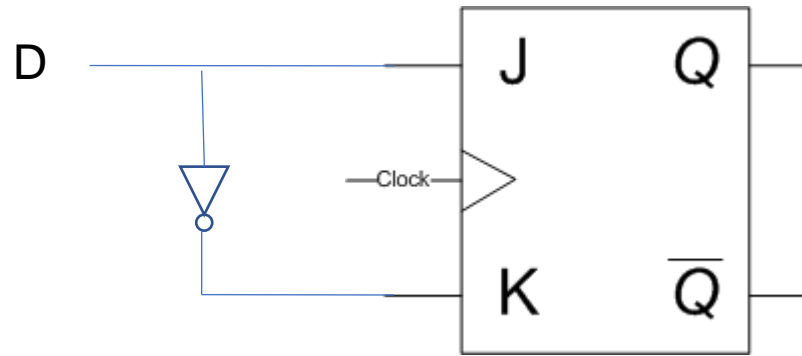

J (= D)	K (=D')	$Q_n$
0	1	0
1	0	0

# T Flip – Flop (Toggle)

 

J (= K)	K (=J)	$Q_n$
0	0	$Q_{n-1}$
1	1	$Q_{n-1}'$