

Combinational Logic Circuits

What is a combinational logic circuit


- A combinational logic circuit is a type of digital circuit whose **output is a pure function of the present input** only.
- Unlike sequential circuit combinational logic state does not have memory element and current state is effect for next state
- **Adders, Subtractors, multiplexer, demultiplexers, encoders and decoders** are the types of combinational log circuits
- **Applications:** ALU (Arithmetic logic unit), Control systems, calculators and inside of computers

Why Adders ?




- CPU of a computer contains an arithmetic logic circuit
- It is a combinational circuit that performs arithmetic operations such as $+$, $-$, \times , \div

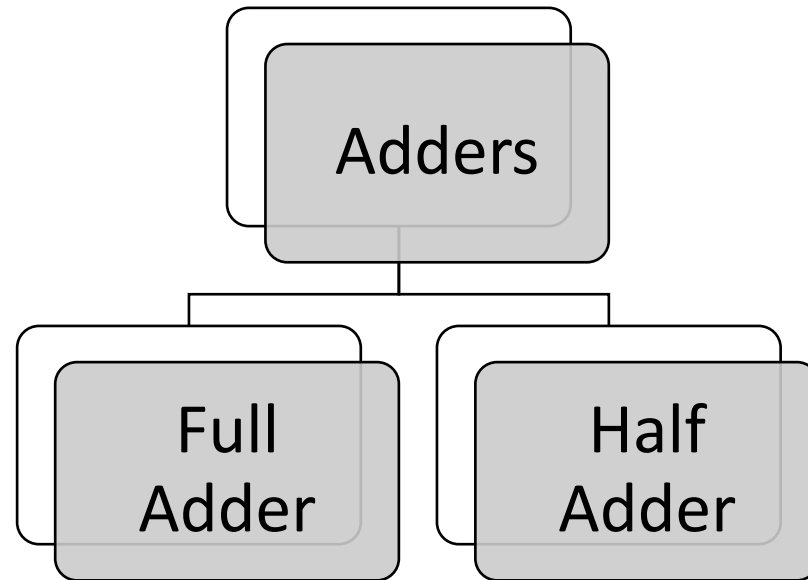- A **adder** is used to performed **binary numbers addition** in a arithmetic logic circuit



Half Adder

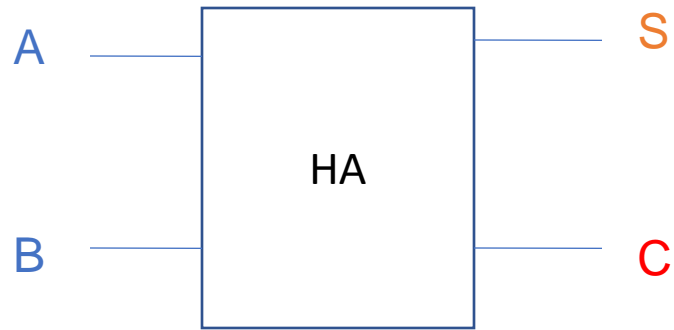


- Use to add two bit binary numbers
- Two bit adder has two inputs and two outputs, sum and carry.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$S = A'B + AB' = A \oplus B$$

$$C = AB$$
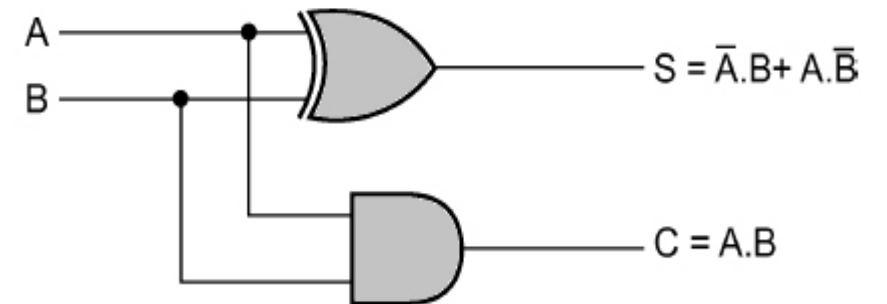
$$\begin{array}{r} 1 \\ +0 \\ \hline 0 \ 1 \end{array} \quad \begin{array}{r} 1 \\ +1 \\ \hline 1 \ 0 \end{array}$$



Full Adder

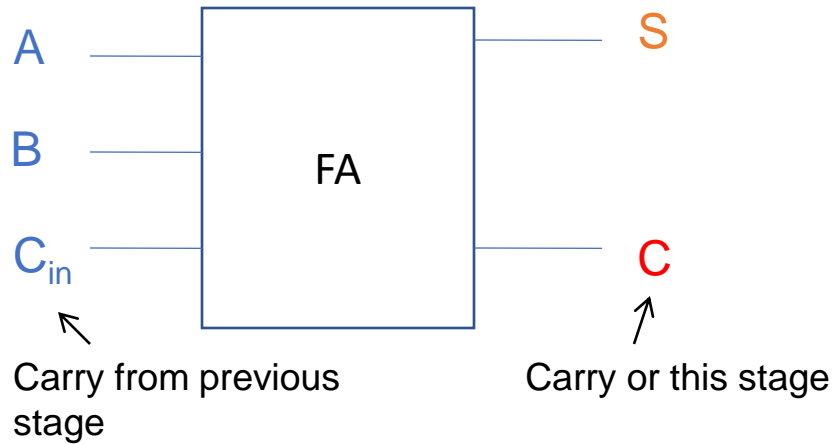

$$\begin{array}{r} 1 \\ 01 \\ +11 \\ \hline 0 \end{array}$$


One that performs the addition of two bits is called a full adder.

C_{in}	A	B	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{array}{r} 0 \\ +0 \\ \hline 0 \\ +0 \\ \hline 0 \end{array} \quad \begin{array}{r} 0 \\ +1 \\ \hline 1 \\ +0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ +1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ +1 \\ \hline 1 \end{array}$$

Diagram illustrating the addition of two bits (0 and 1) using a full adder. The first column shows the addition of 0 and 0, resulting in 0. The second column shows the addition of 0 and 1, resulting in 1. The third column shows the addition of 1 and 1, resulting in 0 and a carry of 1. The final result is 10 (2 in decimal).

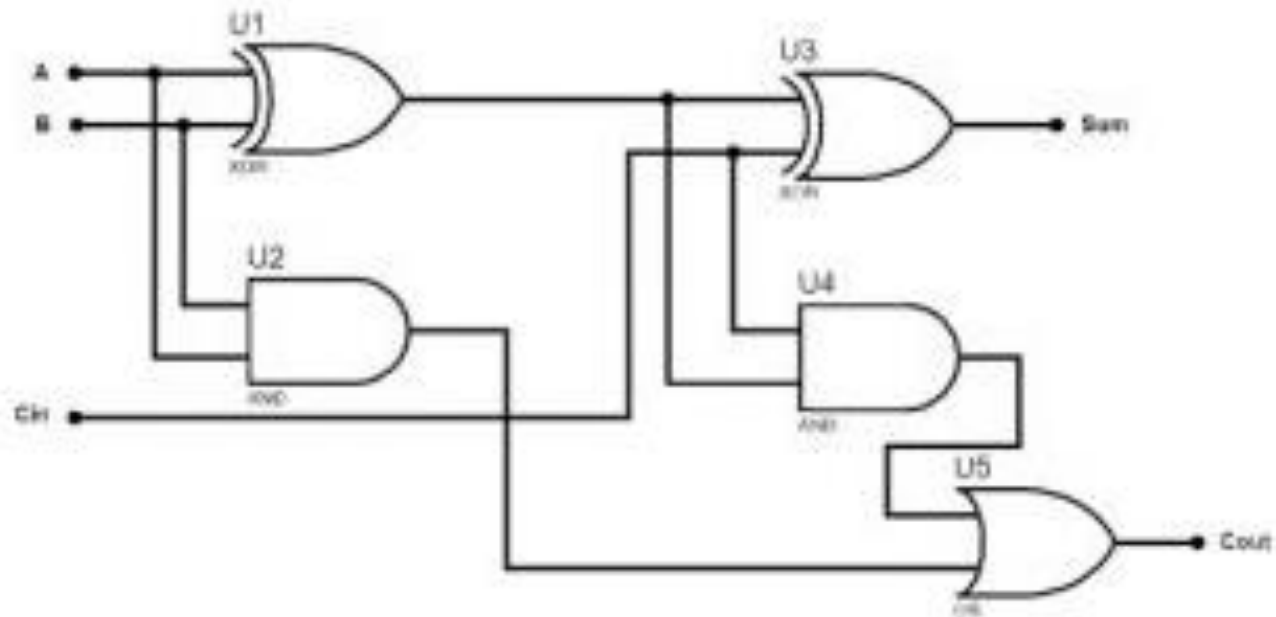

Full Adder using Two Half Adders


Sum of product for sum and carry bits

$$S = A \oplus B \oplus C_{in}$$



$$C = AB + C_{in}(A \oplus B)$$

Multiplexer

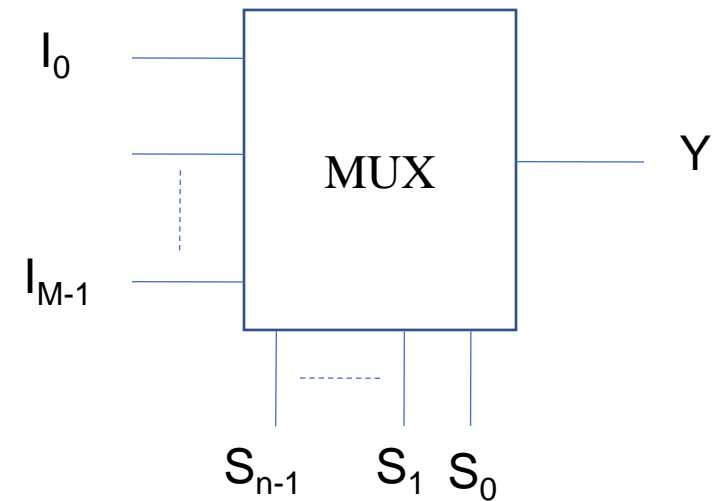- Select one binary signal out from many input lines
- During the process of multiplexing select one particular input into output or multiplexed output
- This process is happening according to selection lines
- The amount of input lines are denoted by “M” and these M number of lines are controlled by “n” selection lines
- $M = 2^n$ M- Input lines n- selection lines
- $n = \log_2 M$




2:1 MUX

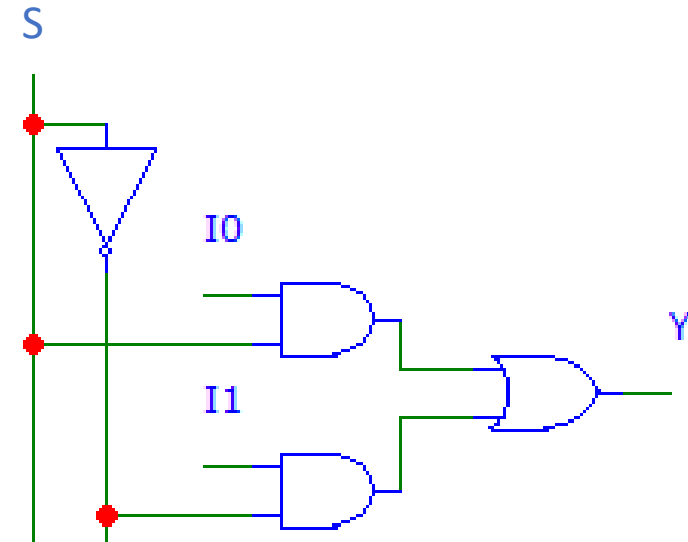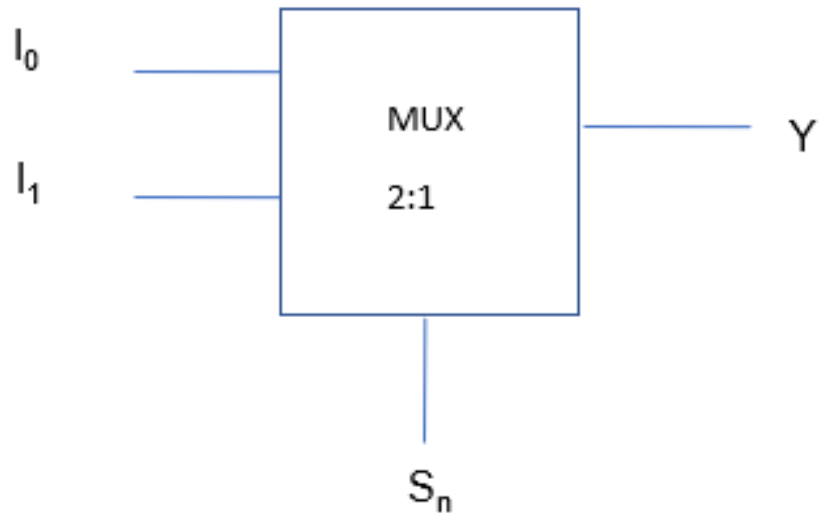


S_n	Y
0	I_0
1	I_1

$$Y = SI_0 + \bar{S}I_1$$


4: 1 MUX

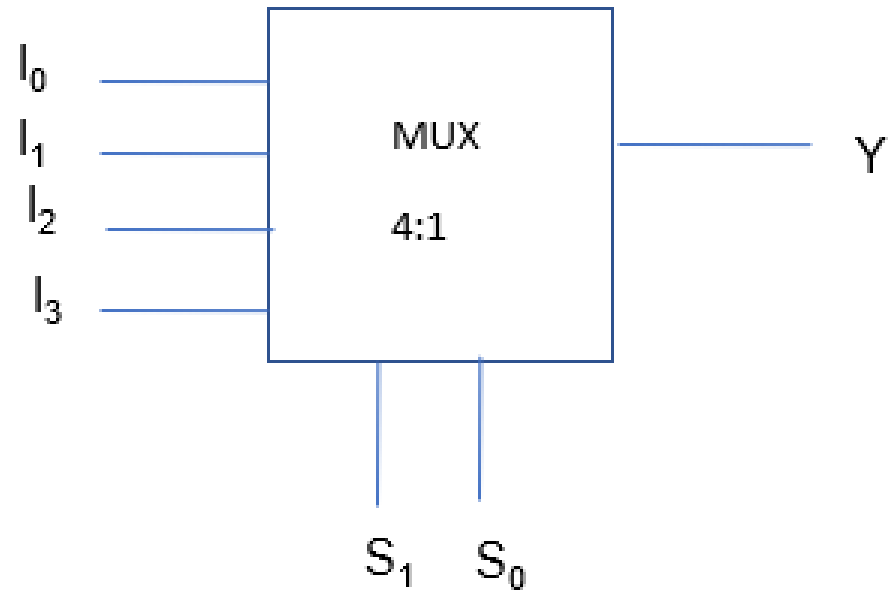

S_0	S_1	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

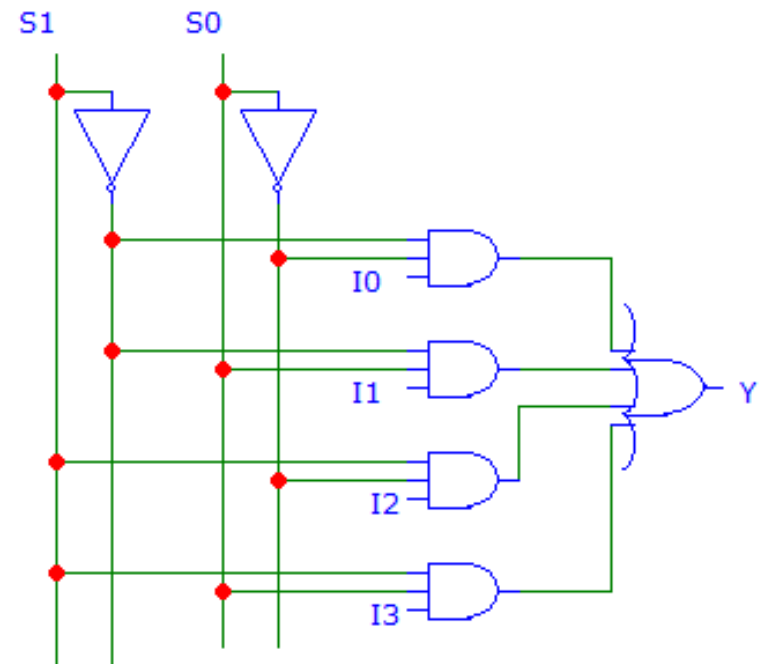

8:1 MUX

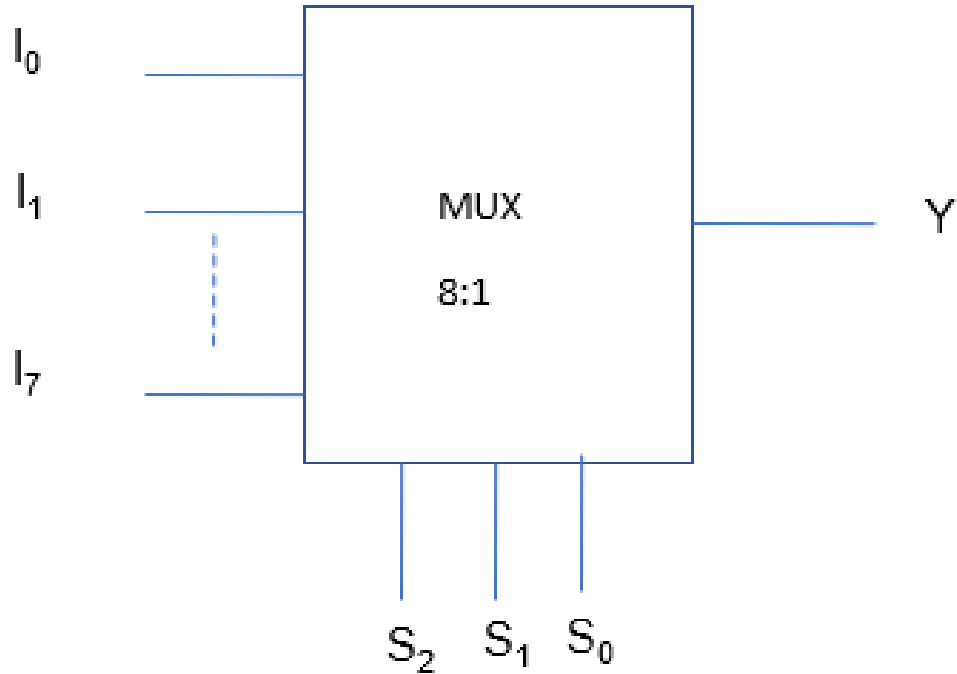


S_0	S_1	S_2	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

- Draw the Logic Diagram
- Implement Mux design of 16:1 Multiplexer

Demultiplexer

- Inverse of multiplexing
- Output the multiple number of output lines by only one input line
- The selection of a particular output line is controlled by a set of selection lines
- There are M output lines controlled by N ($M = 2^N$) selection lines

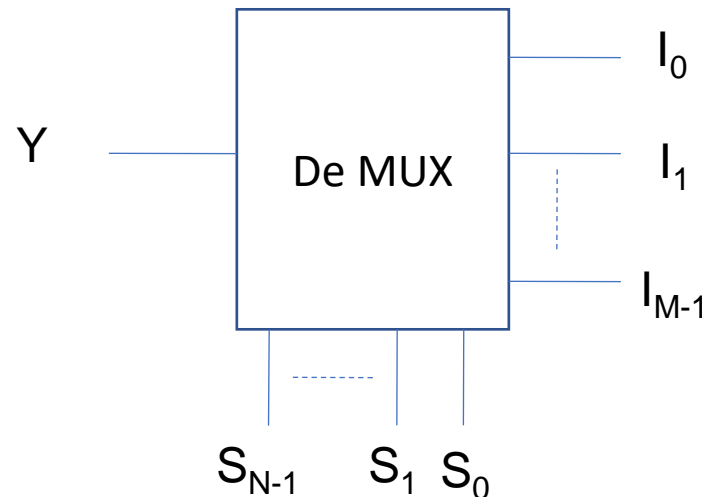

Question 01

- A Fire Alarm system has two sensors to detect smoke or fire in a building. A manual key can also manually breakdown and activate the fire alarm system. When ever
 - If the emergency switch is presses, the alarm will switch on
 - If smoke detecting sensor and fire detecting sensors are activated at the same time the alarm will switch on
 - Either one sensor detect a smoke or fire the alarm will one
- i. Draw the truth table to the given system
- ii. Derive the simplified SOP expression for the output
- iii. Implement the digital circuit of the output alarm
 - a. Only basic logic gates (AND, OR, NOT)
 - b. Only NAND gates
 - d. A suitable Multiplexer

Question 02

- The directors of a company wish to automate the voting procedure at board meetings. When voting, each director has a percentage vote equal to his holdings in the company. A total vote greater than 50% is required to pass a motion. Each director is to have a switch with which to indicate a yes or no vote and a single result lamp is to be turned on if the total vote cast is greater than 50%. The company shares are distributed among the four directors as follows:

- A owns 45%
- B owns 30%
- C owns 15%
- D owns 10%

Design a system to implement the above specification

- i. Draw a truth table
- ii. Implement the system using suitable Multiplexer

Question 03

- An assembly line has 3 failsafe sensors and 1 emergency shutdown switch. The line should keep moving unless any of the following conditions arises.
 - If the emergency switch is pressed, the system shut down
 - If sensor1 and sensor2 are activated at the same time the system shut down
 - If sensor2 and sensor3 are activated at the same time the system shut down
 - If all 3 sensors are activated at the same time the system shut down

Question 04

- A solar energy system has four sensors S1, S2, S3 and S4. The sensor alarm(Y) connected to the heater system will be ON if the following conditions are satisfied:
 - If sensors S3 and S4 are activated at the same time.
 - If at least three of the four sensors are activated at the same time
 - i. Construct a truth table, which describes the input/output relationship
 - ii. Derive the simplified SOP and POS expression for the output
 - iii. Implement the digital circuit of the assembly line using:
 - a. Only basic logic gates (AND, OR, NOT)
 - b. Only NOR gates
 - c. A suitable Multiplexer